

# Hardware Verification

## 2IMF20

Julien Schmaltz

Lecture 02:  
Boolean Functions, SAT, CEC


**TU** / **e**

Technische Universiteit  
**Eindhoven**  
University of Technology

Where innovation starts

# Course content - Formal tools

---

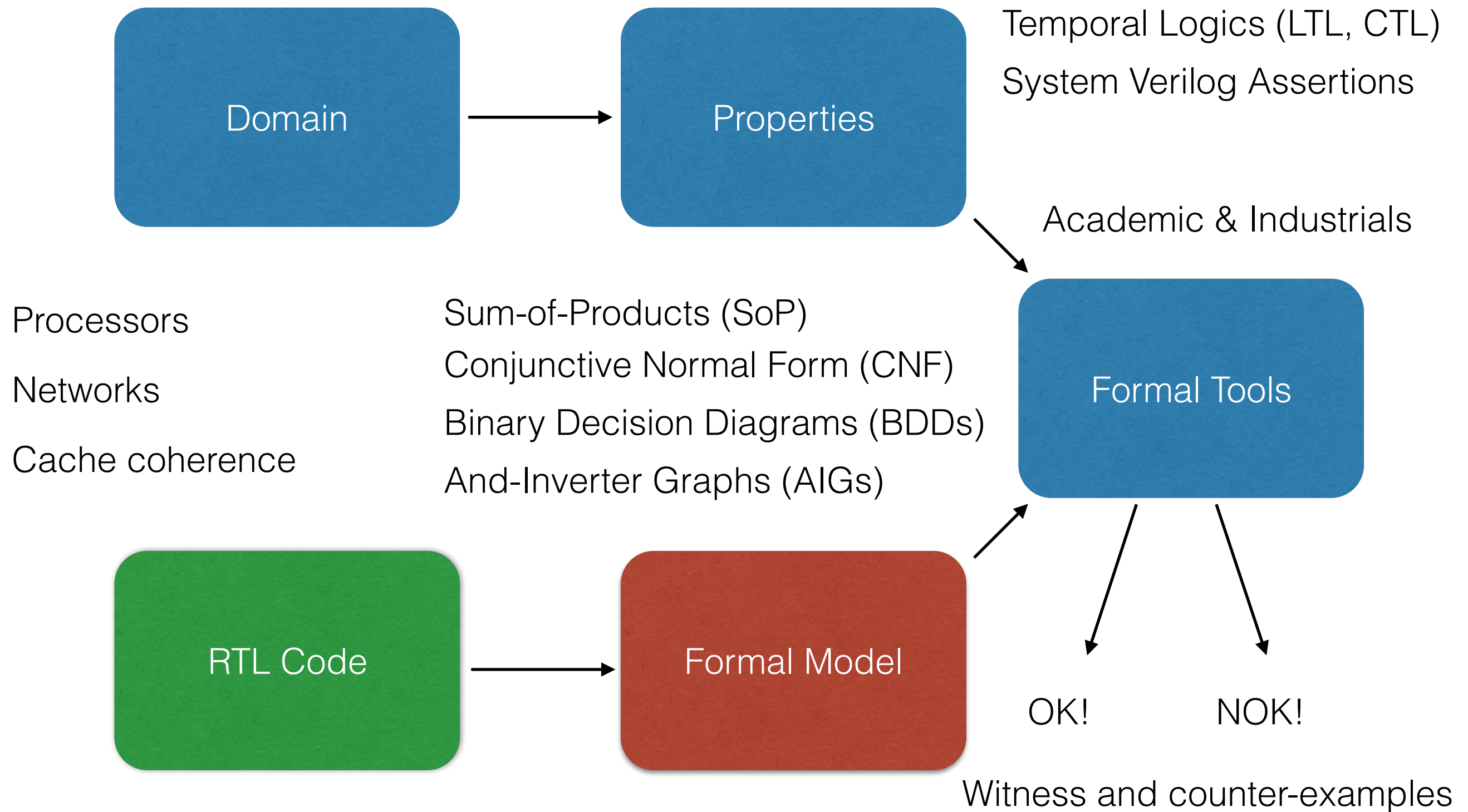



# Goal: Reason about hardware

---

- » Given two circuits: do they compute the same function?
  - » Equivalence checking
  - » Combinatorial and Sequential (next lecture)
  - » Notion of a “Miter” (XOR between outputs)
- » Given a property and circuit: prove that the circuit satisfies the property
  - » Formal Property Verification (FPV) (some lectures from now)
- » In all case, a mathematical representation of the circuit is needed.

# Important concepts

---

- » The need to represent Boolean functions efficiently
- » Different representations have different pros and cons
- » Get to know the main representations used in practice
  - » SoP
  - » DNF and CNF
  - » DAG
  - » AIG
  - » BDD
- » Have a feeling about how good/bad they are
- » Know how they are used in Combinatorial Equivalence Checking
- » Basic principle of SAT solvers
  
- » Note: representing Boolean functions is active research
  - » “Cyclic Boolean Circuits” by Riedel and Bruck, Discrete Applied Mathematics (2012)

# Program for today

---

- » Boolean functions
- » Boolean Satisfiability
- » Combinatorial Equivalence Checking

# Hardware to Formal Representation

---

- » The first step before applying any formal analysis technique is to obtain a formal representation of the design.
  - » from 4 valued logic to Booleans
- » Symbolic Boolean expressions of the wires.
- » Different representations of these expressions
  - » Directed Acyclic Graphs (DAG)
  - » Sum-of-Products (SoP)
  - » Conjunctive Normal Form (CNF)
  - » Disjunctive Normal Form
  - » Binary Decision Diagrams (BDD's)
  - » And-Inverter Graphs (AIG's)

# Boolean functions

---

- Matches most digital hardware, other hardware can be translated into Boolean functions.
- For example, Verilog HDL has 0, 1, and also:  
X (unknown / error)  
Z (not driven, open wire)
- To translate, simply use two 'bits', or Boolean values:  
(False,False): 0  
(False,True): X  
(True,False): Z  
(True,True): 1  
(any other choice will also do)

# Why Boolean functions

---

- For this lecture, we assume two valued logic without X or Z
- As Boolean value, we write:  
0 for False, and 1 for True
- We talk about & for 'and', | for 'or', ! for 'not', etc.  
We can assume we are talking about the logical functions:

$$1 \& 1 = 1, x \& 0 = 0, 0 \& x = 0$$

$$0 | 0 = 0, x | 1 = 1, 1 | x = 1$$

$$!0 = 1, !1 = 0$$



# Expressing Boolean functions:

---

- Data structure should be:
  - Efficient to construct
  - Easy to reason about

# How compact can we store a function?


---

- Truth table:
  - for a Boolean function on  $N$  inputs
  - $2^N$  possible input assignments
  - So,  $2^N$  rows in the truth table
- As most Boolean functions are not “any Boolean function”: we can have smaller representations, most of the time.
- For instance, only represent rows for which an output is 1
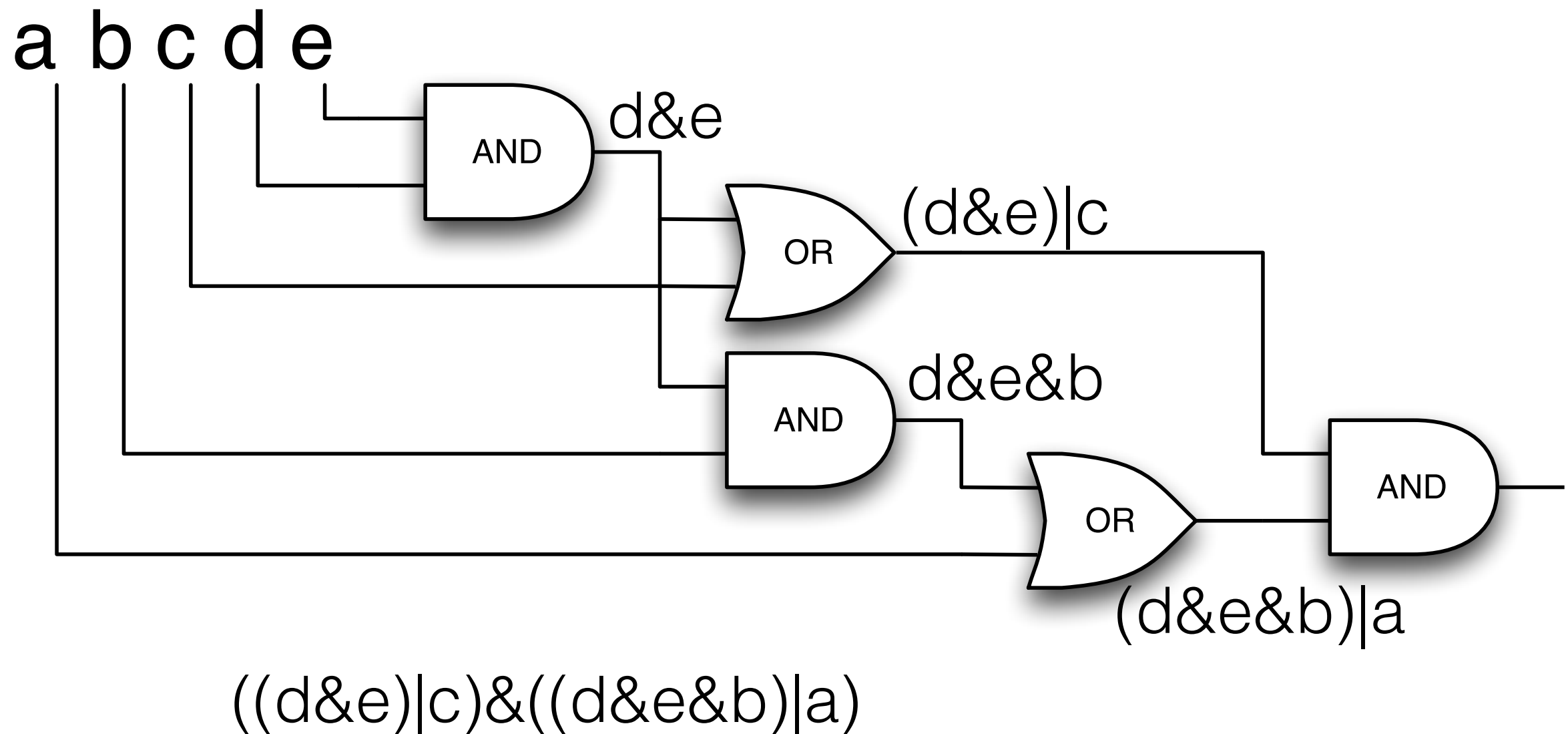
# Directed acyclic graph (DAG)

---


- A directed acyclic graph is a way to represent a Boolean function, it is often used as a synonym for 'circuit'.
- More compact than the function written out!


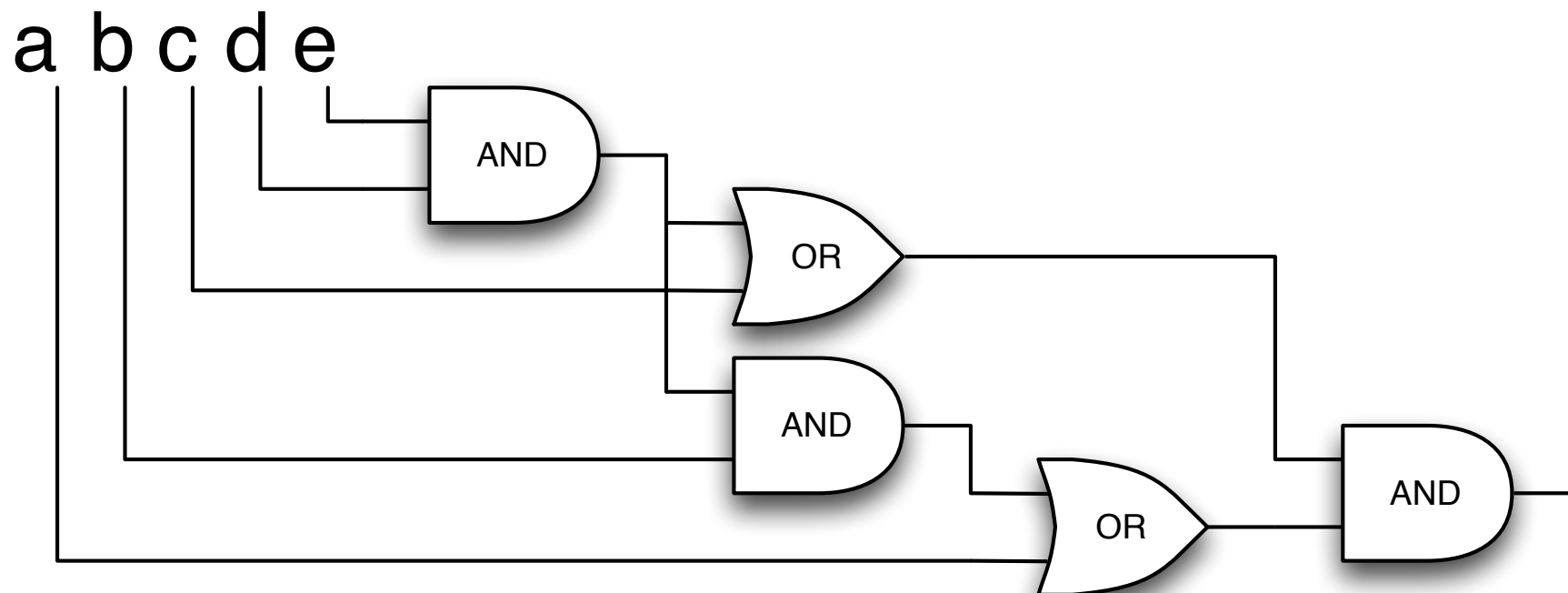
# Directed acyclic graph (DAG)

---


- DAG is a list of 'gates'. A gate at position  $i$  has:
  - a Boolean function assigned to it
  - Each Boolean function gets a list of pointers to other gates, from which it gets its input values
  - Each of those numbers need to point backwards
  - Variables are represented as gates without inputs



# Directed acyclic graph (DAG)

---

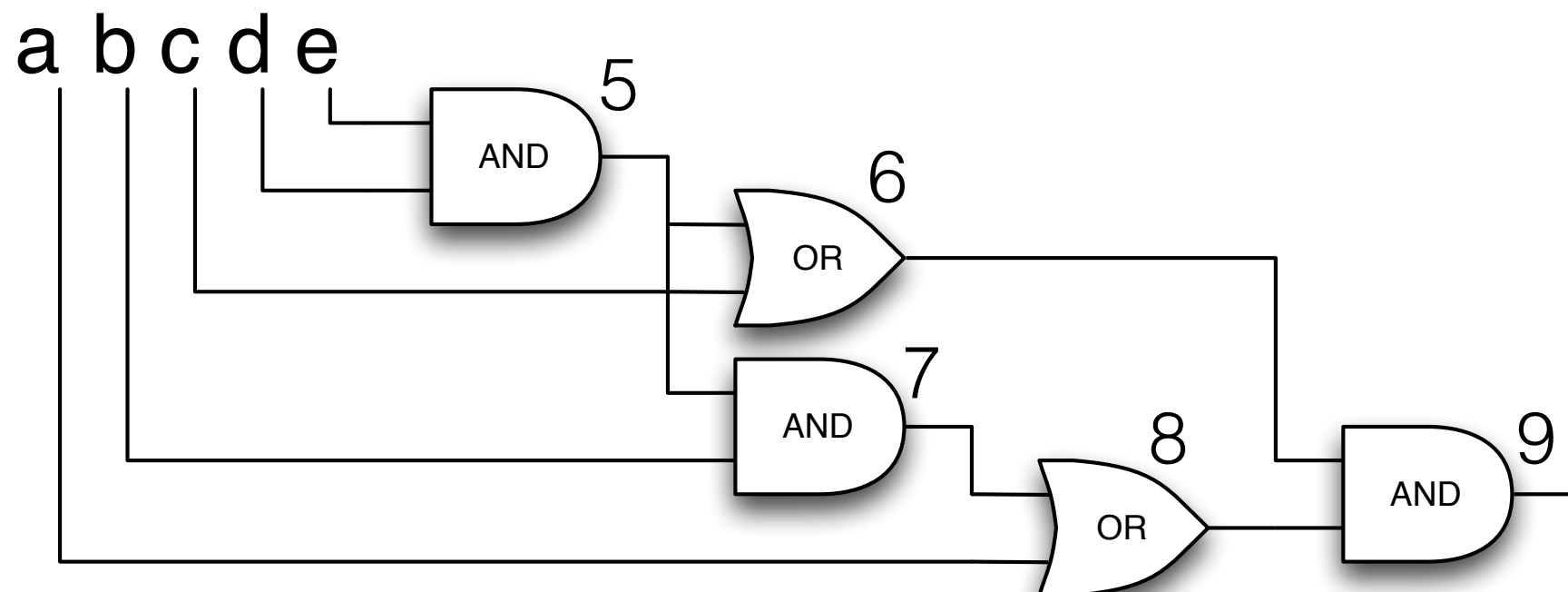- 0: variable "a"
- 1: variable "b"
- 2: variable "c"
- 3: variable "d"
- 4: variable "e"
- 5: and [3,4]
- 6: or [5,2]
- 7: and [5,1]
- 8: or [7,0]
- 9: and [6,8]





# Directed acyclic graph (DAG)


---

- DAG is easy to construct (follows hardware directly)
- Large amount of different gates:
  - makes it hard to write and maintain programs that reason with DAGs
- Alternative: And-Inverter Graph (AIG)
  - Uses just two gates: AND and NOT
 
# And-Inverter Graph (AIG)

---


- Every gate can be converted into a fixed amount of AIG gates


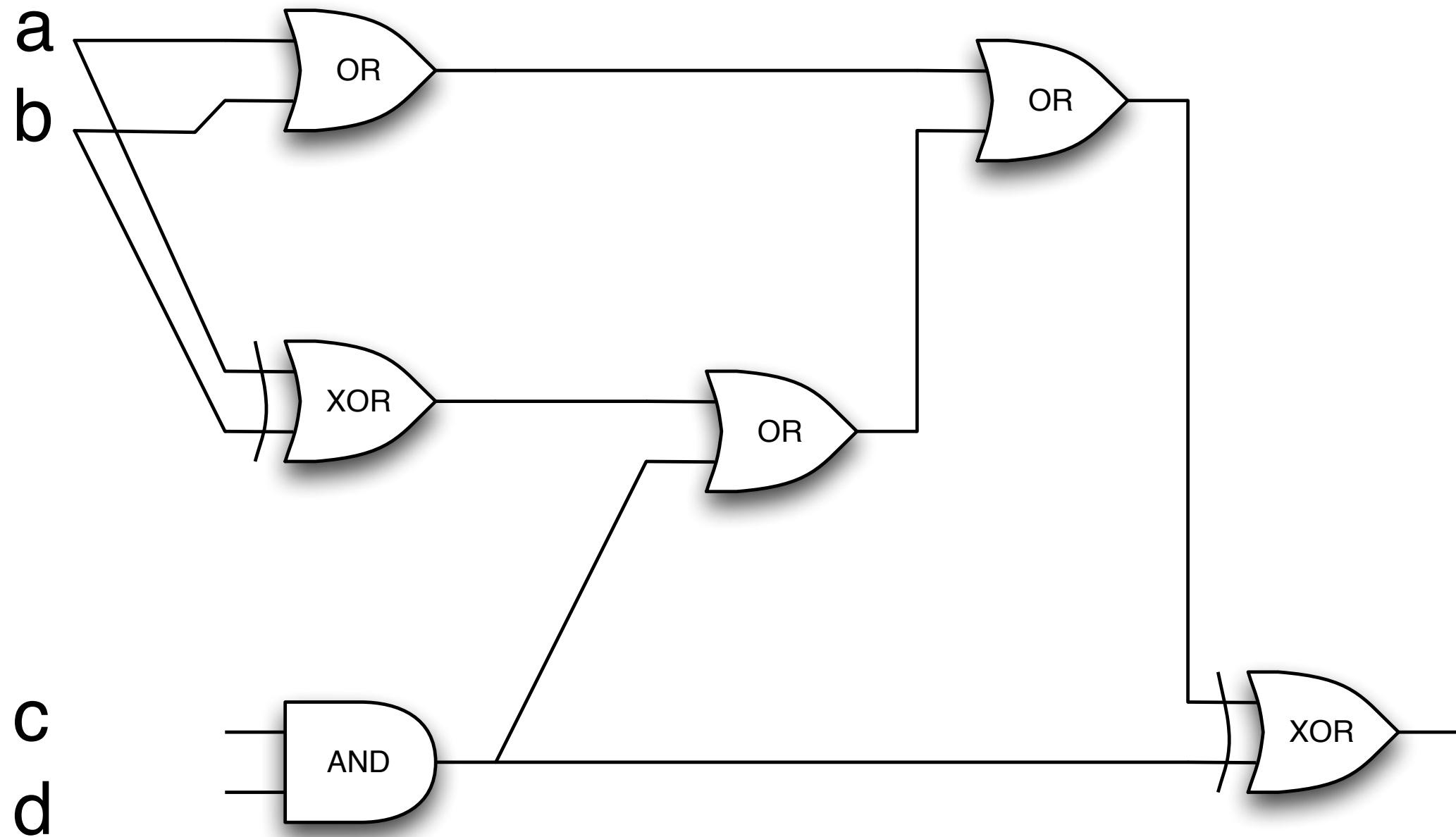
# AIG

---


- Every gate can be converted into a fixed amount of AIG gates


 
# AIG

---


- Every gate can be converted into a fixed amount of AIG gates


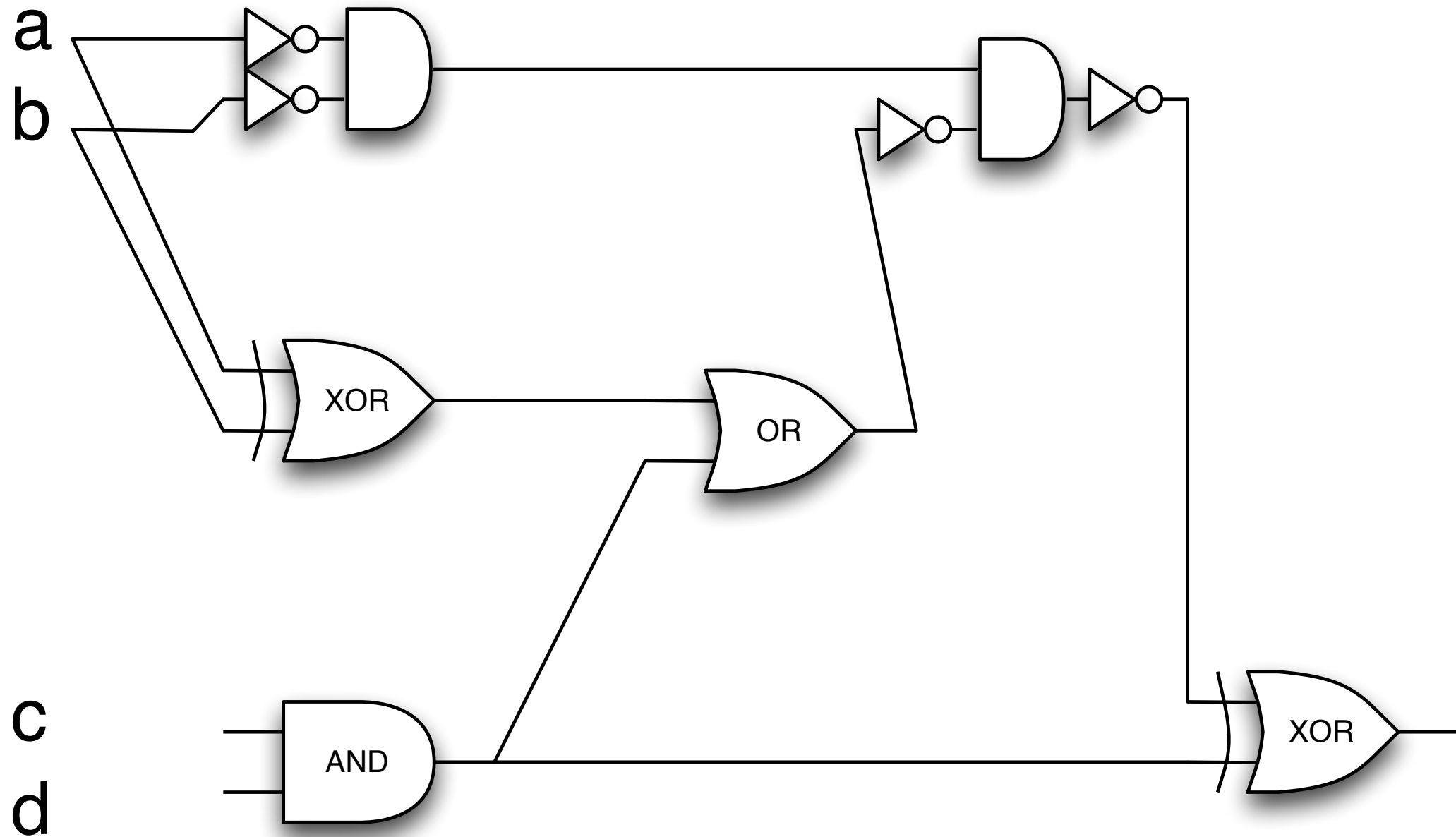
# AIG

---

- Cannot put two inverters between two gates






# AIG

---


- Sometimes, AND gates are the same

 
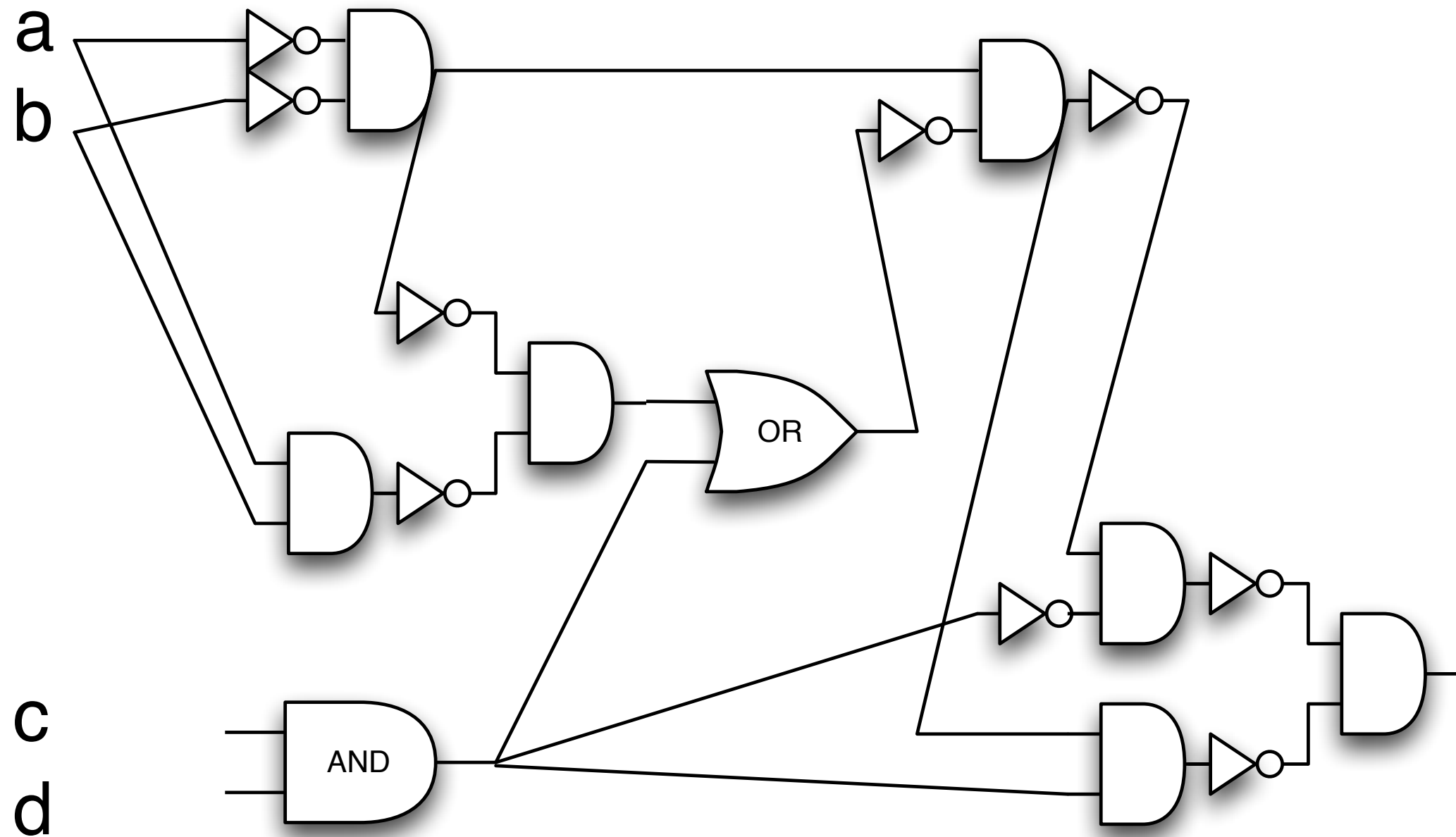
# AIG


---

- We may share AND gates that have the same input


 
# AIG


- Two inverters in a row are removed (not not is identity)


 
# AIG

---

- Conceptually, inverters belong with the next gate



# AIG


---

- AIG storage is really compact:
  - All nodes get even numbers
  - First node, 0, stands for False
  - To negate a node, use its number +1


 
# AIG

- 2 *a*
- 4 *b*
- 6 *c*
- 8 *d*
- 26 *output*
- 10 3 5 *!a&!b*
- 12 2 4
- 14 6 8
- 16 11 13
- 18 17 15
- 20 10 18
- 22 21 15
- 24 20 14
- 26 23 25



# Advantages of AIG

---


- Linear size compared to DAG
- Useful as intermediate structure for synthesis:
  - NAND gate has 4 transistors in CMOS
  - NOT has 2
  - AIG Structure gives good area and clock-speed estimates
  - Example tool that uses AIGs:

ABC, A System for Sequential Synthesis and Verification  
Berkeley Logic Synthesis and Verification Group
 
# Data structures, so far:

---

- DAG
- AIG (Is roughly the same, but with a few conditions)
- Next:  
conjunctive normal form



# Conjunctive normal form (CNF)

---

- Simple grammar:  
CNF = (Disjunction) & CNF  
CNF = (Disjunction)  
CNF = True  
Disjunction = Term | Disjunction  
Disjunction = Term  
Disjunction = False  
Term = Variable  
Term = ! Variable
- Example:  
 $(x \mid y) \& (!z \mid x \mid !y) \& (z \mid -x)$
- Rules:
  - All variables within an disjunction must be unique. Including x and !x: they do not occur in the same disjunction

# Creating CNF

---

- Naive way:  
Procedure for AND and NOT, translate from AIG
- AND is trivial:  
AND of  $[(a|b|c)\&(d|e|f)\&(i|j)] [(g|h)\&(i|j)]$  becomes:  
 $[(a|b|c)\&(d|e|f)\&(g|h)\&(i|j)]$  or even  
 $[(a|b|c)\&(d|e|f)\&(i|j)\&(g|h)\&(i|j)]$
- NOT is problematic: goes from CNF to DNF back to CNF  
 $[(a|b|c)\&(d|e|f)\&(i|j)]$  becomes:  
 $[(-a|-d|-i)\&(-a|-d|-j)\&(-a|-e|-i)\&(-a|-e|-j)\&(-a|-f|-i)\&(-a|-f|-j)$   
 $\&(-b|-d|-i)\&(-b|-d|-j)\&(-b|-e|-i)\&(-b|-e|-j)\&(-b|-f|-i)\&(-b|-f|-j)$   
 $\&(-c|-d|-i)\&(-c|-d|-j)\&(-c|-e|-i)\&(-c|-e|-j)\&(-c|-f|-i)\&(-c|-f|-j)]$
- **This is not going to scale!**



# Another way to create CNF - AND

---

- » Consider  $C = \text{AND}(A, B)$
- » Goal: create CNF formula  $f$  such that  $f(a, b, c) == (C = A \& B)$
- » if  $A$  is false, then  $C$  is false
  - » “ $\neg A$  implies  $\neg C$ ”, logically equivalent to the clause  $A \mid \neg C$
  - » similarly for  $B$ :  $B \mid \neg C$
- » If  $A$  and  $B$  are true, then  $C$  is true
  - » “ $A \& B$  implies  $C$ , logically we get  $\neg A \mid \neg B \mid C$ ”
- » Finally, the encoding for an AND-gate is:
  - »  $(A \mid \neg C) \& (B \mid \neg C) \& (\neg A \mid \neg B \mid C)$
- » Linear expansion: 3 clauses for each AND-gate

# Another example: XOR

---

- » Consider  $C = \text{XOR}(A, B)$
- » Goal: create CNF formula  $f$  such that  $f(a, b, c) == (C = A \text{ XOR } B)$
- » if  $A$  and  $B$  are false, then  $C$  is false
  - » “ $\neg A$  and  $\neg B$  implies  $\neg C$ ”, logically equivalent to  $A \vee B \vee \neg C$
- » If  $A$  is true and  $B$  is false, then  $C$  is true
  - » “ $A \ \& \ \neg B$  implies  $C$ ”, logically we get  $\neg A \vee B \vee C$
  - » Symmetric case:  $A \vee \neg B \vee C$
- » If  $A$  and  $B$  are true, then  $C$  is false
  - » “ $A \ \& \ B$  implies  $\neg C$ ”, logically we get  $\neg A \vee \neg B \vee \neg C$
- » Finally, the encoding for an XOR-gate is:
  - »  $(A \vee B \vee \neg C) \ \& \ (\neg A \vee B \vee C) \ \& \ (A \vee \neg B \vee C) \ \& \ (\neg A \vee \neg B \vee \neg C)$


# CNF

---

- Like AIG, CNF is linear in the size of the original DAG, but only if we add 'helper' variables.
- CNF is used as the internal structure of most SAT solvers, including MiniSAT
- CNF is the input format in the SAT competition, and in many of its variations
- Some optimisations are easier on AIGs, so tools built on SAT solvers sometimes translate Boolean primitives to AIG to CNF, for example: Boolector. Other tools translate Boolean primitives to CNF directly, such as Yices

# CNF: typical optimisations

---

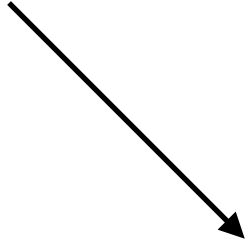- Never have disjunctions with one variable:  
 $(a \mid b \mid v10) \& (-a \mid -v10) \& (-b \mid -v10) \&$   
 $(-a \mid -b \mid v12) \& (a \mid -v12) \& (b \mid -v12) \&$   
 $(-c \mid -d \mid v14) \& (c \mid -v14) \& (d \mid -v14) \&$   
 $(v10 \mid v12 \mid v16) \& (-v10 \mid -v16) \& (-v12 \mid -v16) \& (-v10)$ 
- $-v10$  is necessarily True, so  $v10$  is False  
 $(-a) \& (-b) \&$   
 $(-a \mid -b \mid v12) \& (a \mid -v12) \& (b \mid -v12) \&$   
 $(-c \mid -d \mid v14) \& (c \mid -v14) \& (d \mid -v14) \&$   
 $(v12 \mid v16) \& (-v12 \mid -v16)$
- New single variable disjunctions:  $a$  and  $b$  are False  
 $(-v12) \& (-v12) \&$   
 $(-c \mid -d \mid v14) \& (c \mid -v14) \& (d \mid -v14) \& (v12 \mid v16) \& (-v12 \mid -v16)$
- New single variable disjunctions:  $v12$  is False  
 $(-c \mid -d \mid v14) \& (c \mid -v14) \& (d \mid -v14) \& (v16)$
- New single variable disjunctions:  $v16$  is True

# CNF: typical optimisations (2)

---

- Remove strictly larger disjunctions:  
 $(a \mid b)$  implies  $(a \mid b \mid c)$ , so  $(a \mid b \mid c)$  is redundant.  
Replace  $(a \mid b) \ \& \ (a \mid b \mid c)$  by  $(a \mid b)$ .
- If a variable only occurs positively/negatively, remove it:  
 $(-c \mid -d \mid v14) \ \& \ (c \mid -v14)$   
becomes:  $(c \mid -v14)$  by assigning  $d$  to False,  
which then becomes: True  
by assigning  $c$  to True (or  $v14$  to False)
- If a variable occurs twice, positively in one clause, and negatively in another clause, we can merge these clauses:  
 $(-c \mid -d \mid v14) \ \& \ (a \mid b \mid c)$  becomes  $(a \mid b \mid -d \mid v14)$   
(if  $c$  does not occur elsewhere!)
- Recall the rule:  
Never have  $-x$  and  $x$  in one disjunction (it is always True)

# CNF: summary


---

- Can be constructed in linear size if we allow for additional variables
- Easy to reason with
- Common file format for many purposes
 
# Data structures, so far:

---

- DAG
- AIG
- CNF
- Next: binary decision diagram



# Binary Decision Diagram (BDD)

---

- Canonical form exists:  
two structures are equivalent if they are equal.
- Drawback: usually very large structures




# Binary Decision Diagram (BDD)

---



- DAG with the following nodes
  - Constant 0
  - Constant 1
  - If-then-else with a variable as condition
- Rules for Ordered-BDD:
  - Variables are ordered, gates must occur in that order:  
if  $a > b > c > d > e > f$ , then the “if  $c$  then .. else ..” gate can contain gates with  $b$  and  $a$ , but not with  $d$ ,  $e$  and  $f$ .
- Rules for Reduced-BDD:
  - All gates must be different (no two gates with the same variables and inputs, e.g. “if  $x$  then  $y$  else  $z$ ”)
  - A gate cannot have the same “then” and “else” clause
- Theorem: if a BDD is Reduced AND Ordered, it is canonical.

# Binary Decision Diagram (BDD)

- AIG node 10:

 


- AIG node 12:

  


# Binary Decision Diagram (BDD)



- AIG node 11:

 

- AIG node 13:

 


- AIG node 16:

  


# Binary Decision Diagram (BDD)




- AIG node 14:

 

- AIG node 15:

 


- AIG node 17:

   


# Binary Decision Diagram (BDD)


- AIG node 18:

 

- AIG node 15:


 


- AIG node 17:

 


# Binary Decision Diagram (BDD)


- AIG node 18:

  

- AIG node 15:

 

- AIG node 17:

 

# Binary Decision Diagram (BDD)


---

- Canonical form: ROBDD
- AND of two BDDs introduces blowup
- Used in model checkers
  - Usually SAT-based (CNF/AIG) model checking is faster
  - Not always
- We will come back with more details about BDD's later when we will talk about Symbolic Model Checking
 
# Data structures, so far:

---

- DAG
- AIG
- CNF
- BDD
- Up next: Sum of products





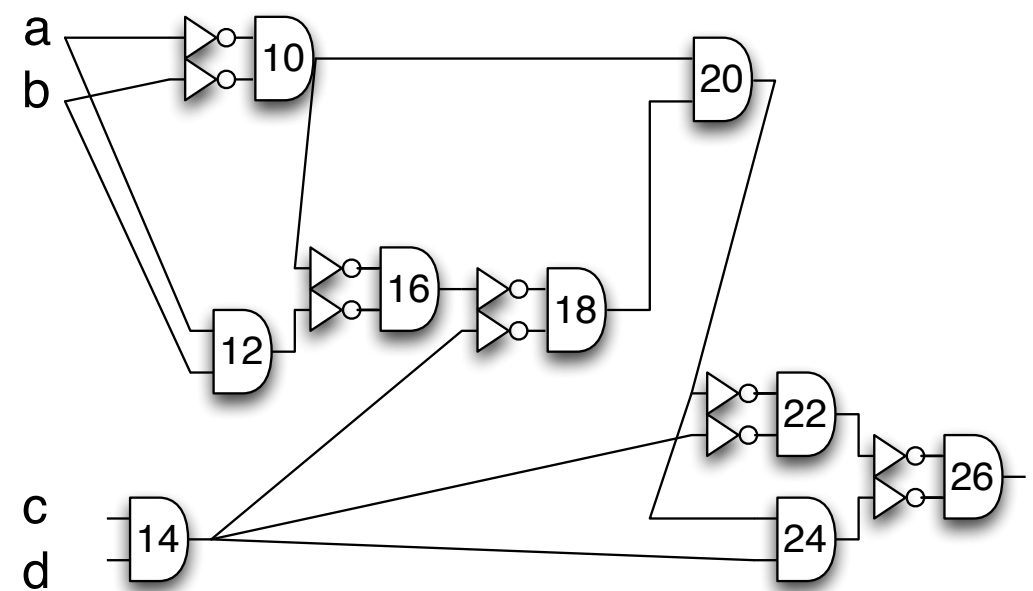
# Sum of products

---

- A lot like CNF, but operations are chosen such that a SOP is canonical.
- Most common choice of operations: AND (product) + XOR (sum)
- AND is innermost, XOR is outermost operation



# Sum of products

---

- not a: True XOR a

AND of {}

AND of {a}

- (True XOR a) & (True XOR b)

=

True & True

XOR

True & b


XOR

a & True

XOR

a & b


= True XOR a XOR b XOR a&b

 
 
# Sum of products (SOP)

---


- Unlike CNF, do not introduce helper variables
- Negation of  $x$  is simply “ $x$  XOR 1”
- SOP is canonical, if AND- and XOR- clauses are considered as sets:
  - Sort variables within AND clause, no duplicates
  - Sort variable-sets within XOR clause, no duplicates
- AND of two SOPs introduces blowup



# Sum of products (SOP)

---

 
- 10: True XOR a XOR b XOR a&b  
12: a&b  
11: a XOR b XOR a&b  
13: True XOR a&b  
16: True&a XOR True&b XOR True&a&b  
XOR a&b&a XOR a&b&b XOR a&b&a&b  
= a XOR b XOR a&b XOR a&b XOR a&b XOR a&b  
= a XOR b  
17: True XOR a XOR b  
14: c&d  
15: True XOR c&d  
18: True XOR a XOR b XOR  
c&d XOR c&d&a XOR c&d&b


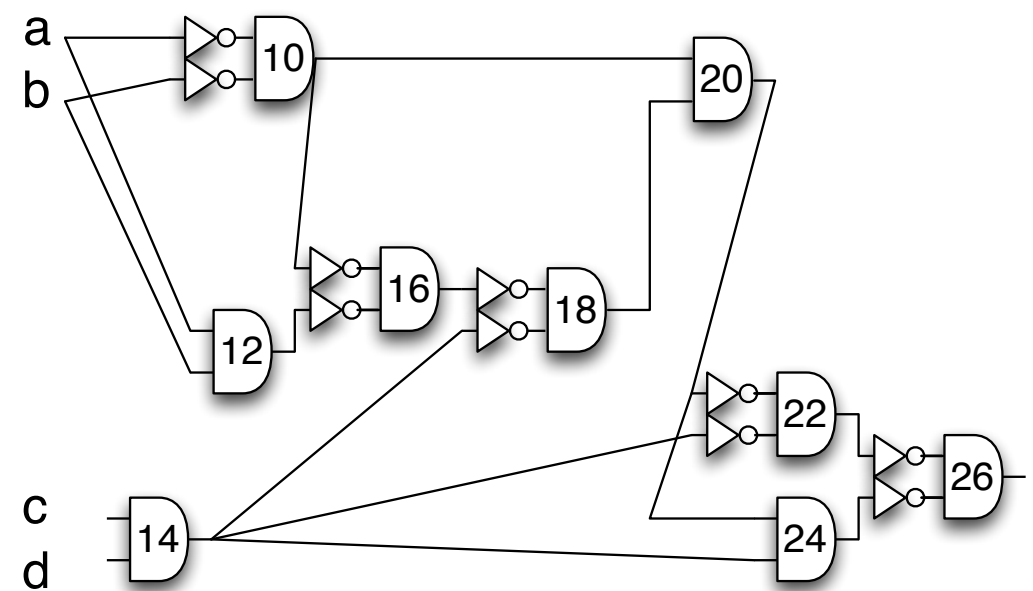
# Datastructures, so far:



---

- DAG
- AIG
- CNF
- BDD
- SOP
- Up next: AIG (again!)



# AIGs vs. SoP

---

  

# AIGs vs. BDDs

---

- » AIGs always size proportional to input
- » BDDs always exponential size for some cases
  - (e.g. multiplier circuits)

# SAT solving

---

- » Once we have Boolean functions, we can do SAT solving.
  - » This is an NP-Hard problem, but efficient in practice
  - » At the basis of almost all modern FV methods.
- 
- » At the next lecture, we will go through the basic algorithm for SAT solving.



# CEC with SoP

---

- » SoP is a normal form
- » CEC obtained by normalising expressions to SoP
- » Then check for syntactic equality

# CEC with BDDs

---

- » ROBDDs is a normal form.
- » Compute the two ROBDDs.
- » Check for syntactic equality.

# CEC with SAT and CNF

---

- » Take two circuits
  - » Create a CNF representation of each one of them
  - » XOR all outputs pairwise
  - » Assert one XOR output is 1
- 
- » Look at code skeleton for assignment 1

# CEC with AIGs



---

- » Step 1: random simulation
- » Step 2: build AIG
- » Step 3: SAT sweeping

(slides taken from Sean Weaver, see course webpage)


# Equivalence Checking

---

  


# Another example (1)

---

 


# Another example (2)

---

 


1 nand-gate to start

 


# Another example (3)

---

 


1 or gate

 




# Another example (3)

---

 


1 nand gate

 


# Another example

---

 

finally 1 or gate with negated inputs

 

# AIGs

---

## » Pros



- simple to build and manipulate
- unifying among synthesis, verification, technology mapping
- compact representation

## » Cons


- structurally not efficient (see FRAIG)
- non canonical

# Equivalence Checking

---

 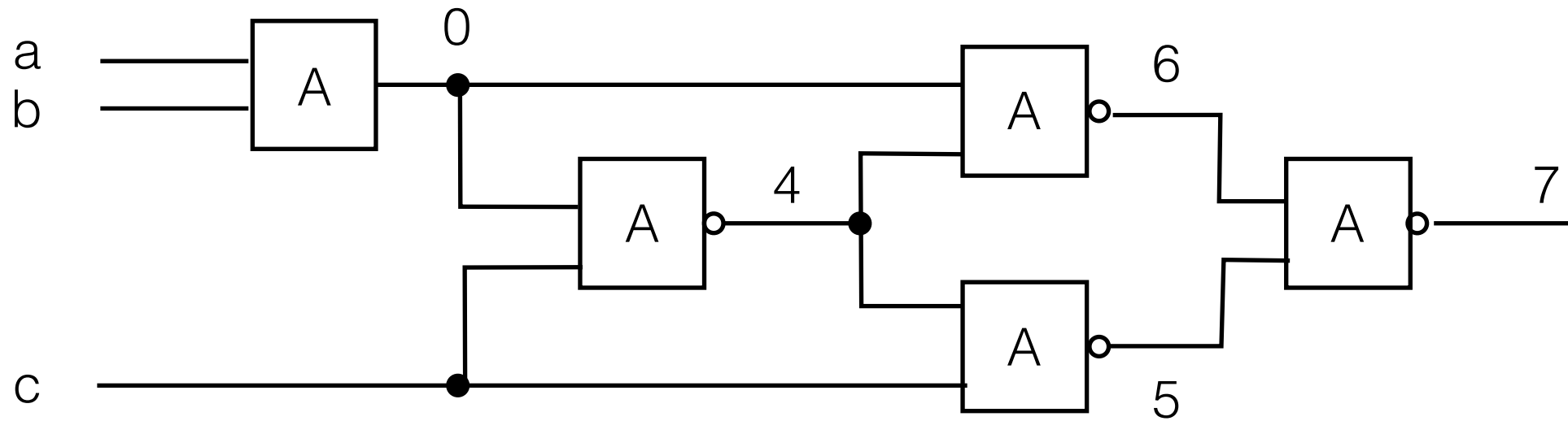


# Random Simulation (1)

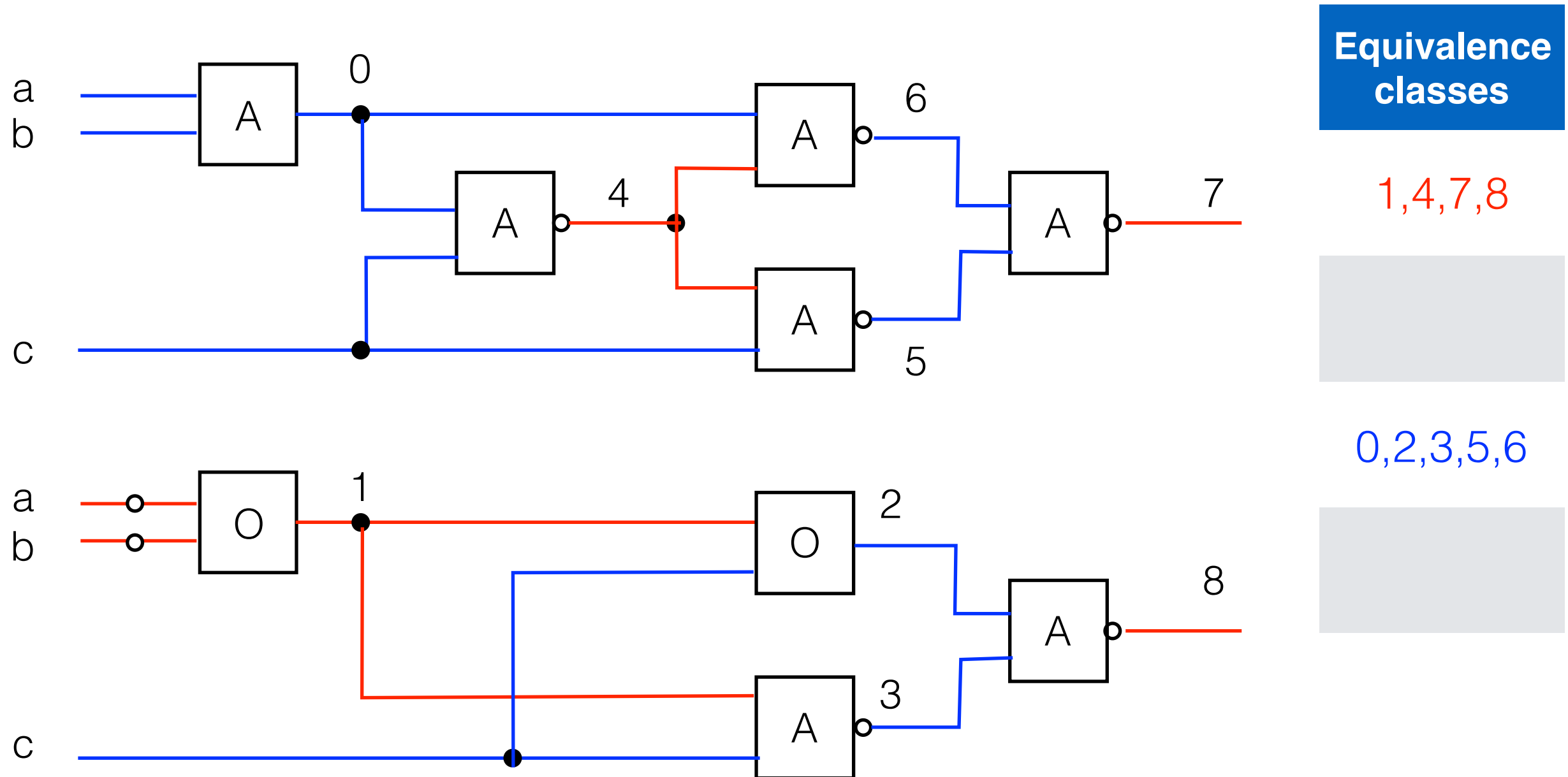


Random Vector: assign T to all inputs.  $a = b = c = T$

# Random Simulation (2)

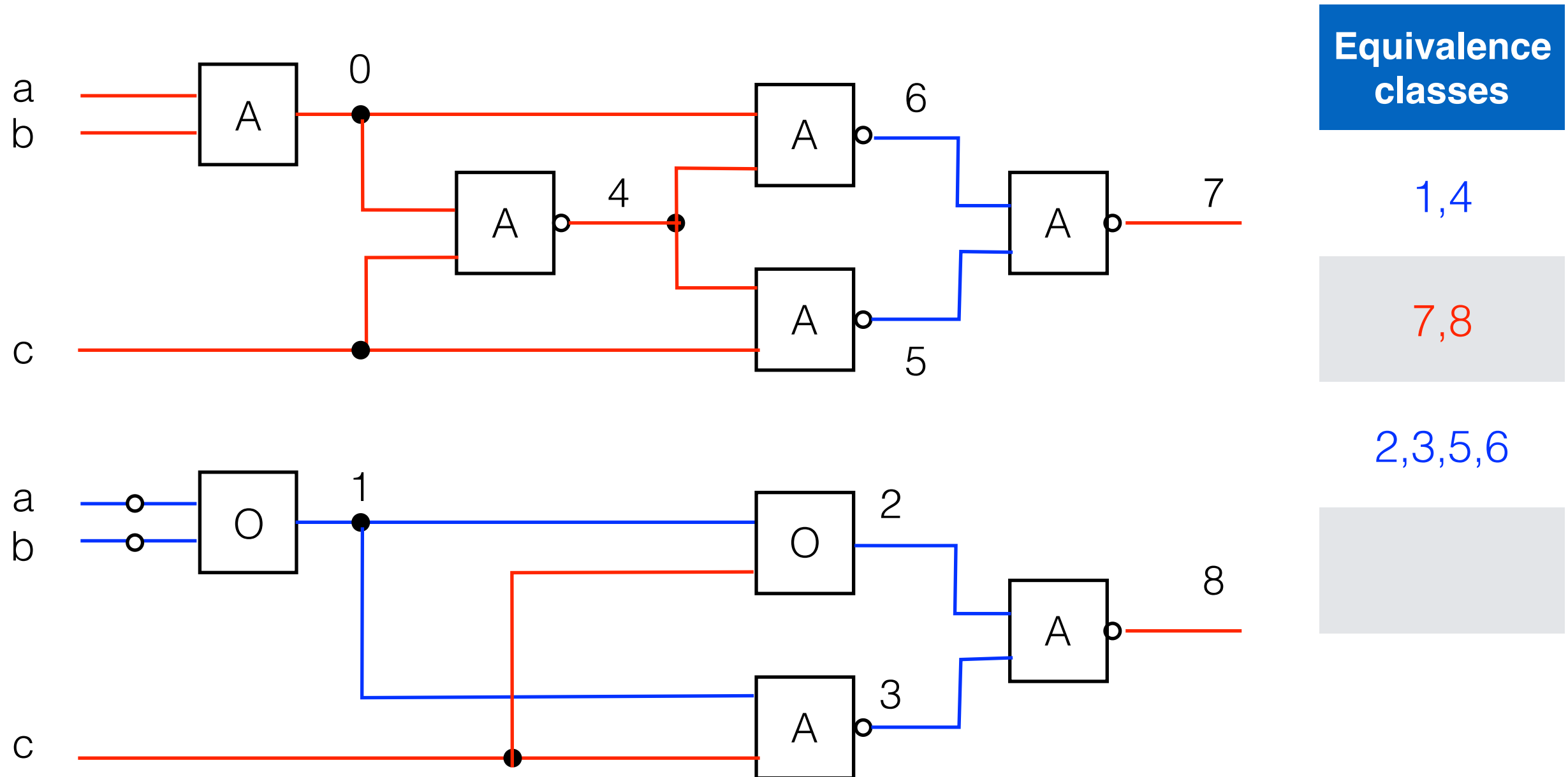


Random Vector: assign F to all inputs.  $a = b = c = \textcolor{red}{F}$

# Random Simulation (3)

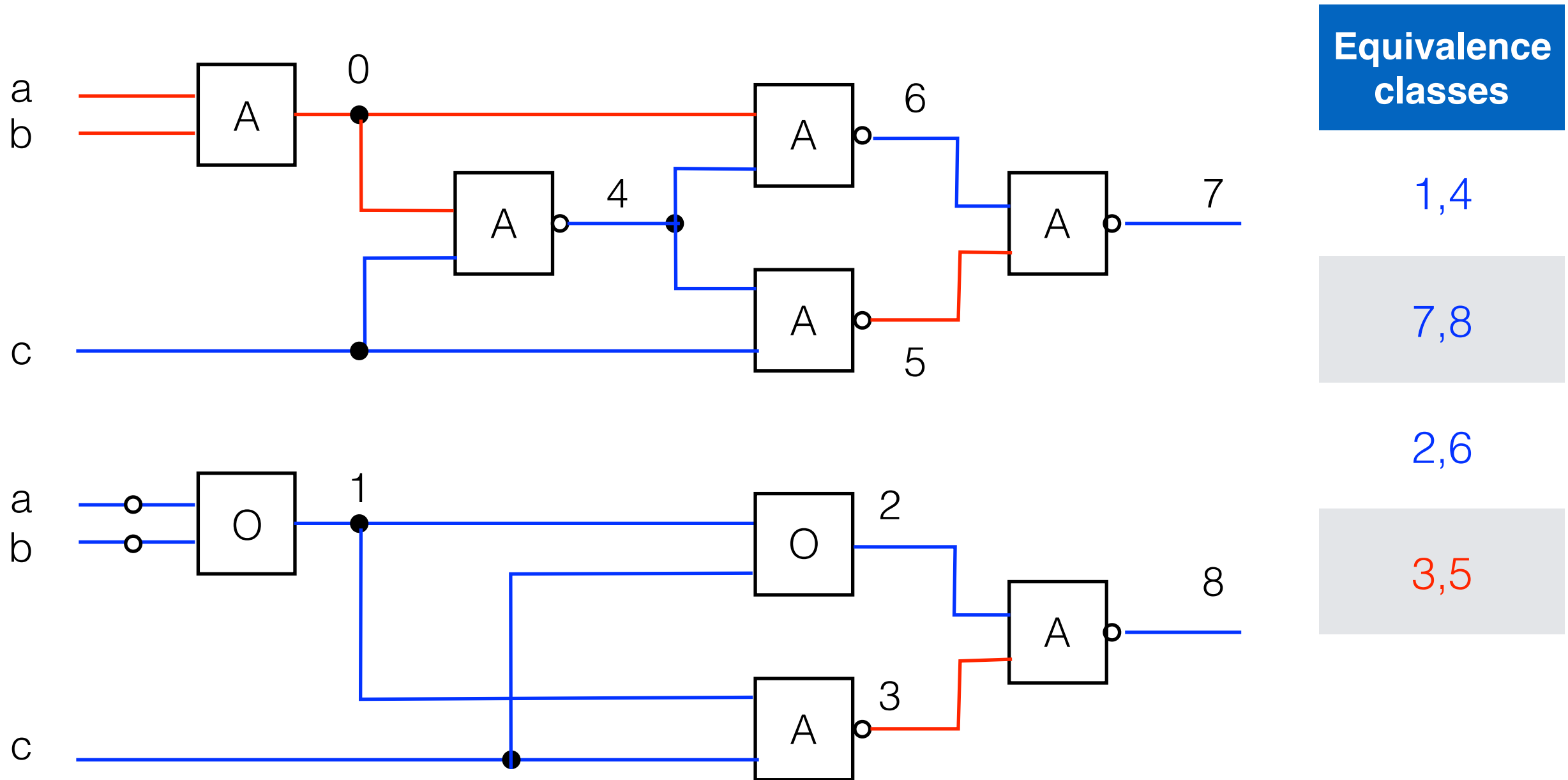

Random Vector:  $a = b = \text{F}$  and  $c = \text{T}$

# Random Simulation (4)


 


Random Vector:  $a = b = \text{blue } T$  and  $c = \text{red } F$





# AIG (1)

---

  


# AIG (2)

---

  


# AIG (3)

---

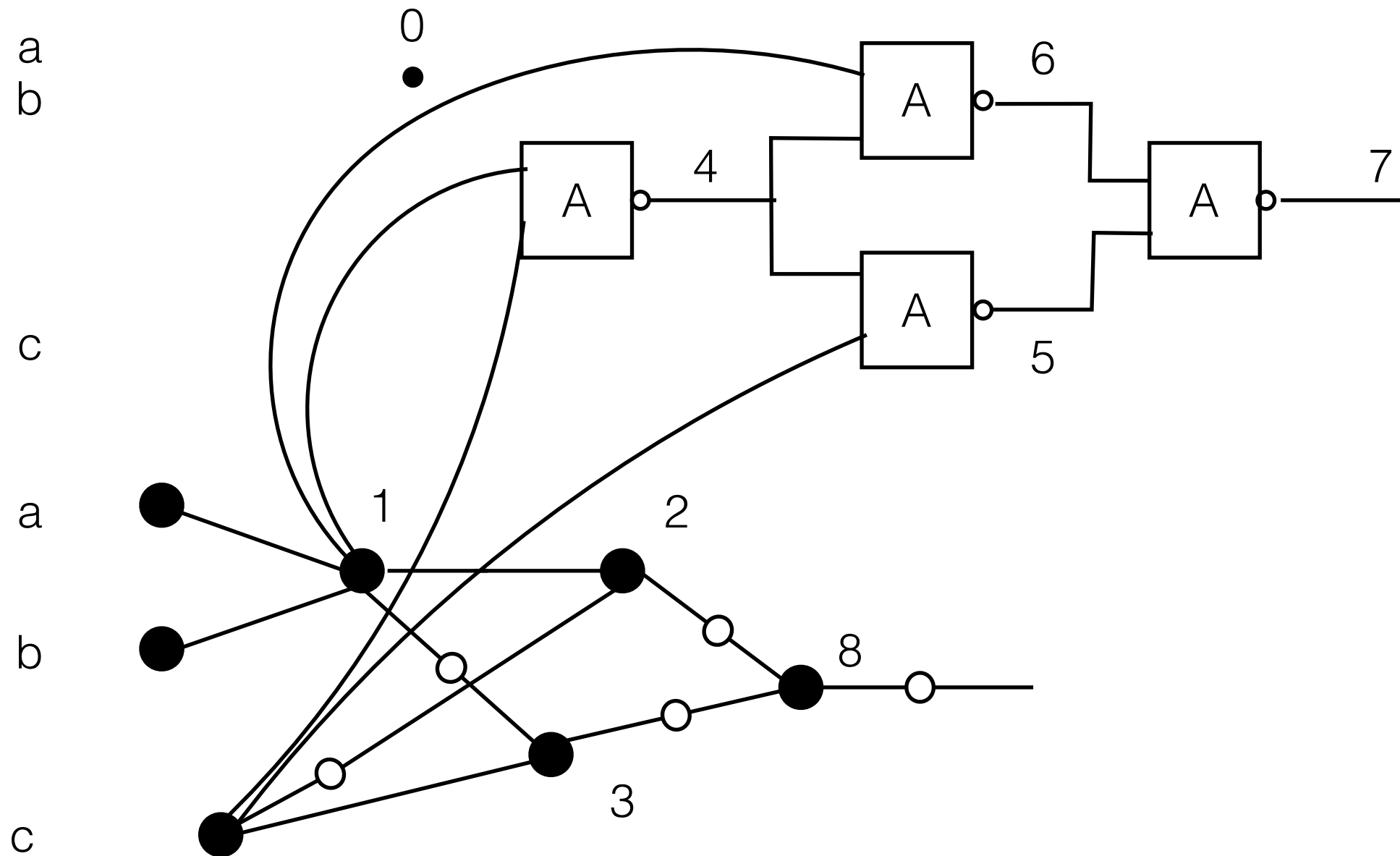

# AIG (4)


---

 




# AIG (5)

---

 

# SAT Sweeping (1)

 

Equivalence classes

7,8


2,6

3,5

SAT solver: 3 = 5

$$\neg(a \wedge b) \wedge c = \neg((a \wedge b) \wedge c) \wedge c$$

# SAT Sweeping (2)

 

Equivalence classes

7,8

2,6


3,5

SAT solver:  $3 = 5$

Merge nodes 3 and 5



# SAT Sweeping (3)

 

Equivalence classes


7,8

2,6

3,5

SAT solver:  $2 = 6$

# SAT Sweeping (4)

 

Equivalence classes

7,8


2,6

3,5

SAT solver:  $2 = 6$

Merge nodes 2 and 6

# SAT Sweeping (5)

 

Equivalence classes

7,8

2,6

3,5

7 structurally hashes to 8  
So, circuits are equivalent

# FRAIGS

---

- » Instead of SAT sweeping
- » On-the-fly build a Functionally Reduced AIG
  - » Structural hashing, one or two-levels
  - » Simulation with test-vectors
  - » Call SAT for possibly equivalent nodes
  - » Keep functional equivalent nodes, but re-use just one of them

# Simple exercises to practice

---

- » See reader (Chapter 2) on the website